
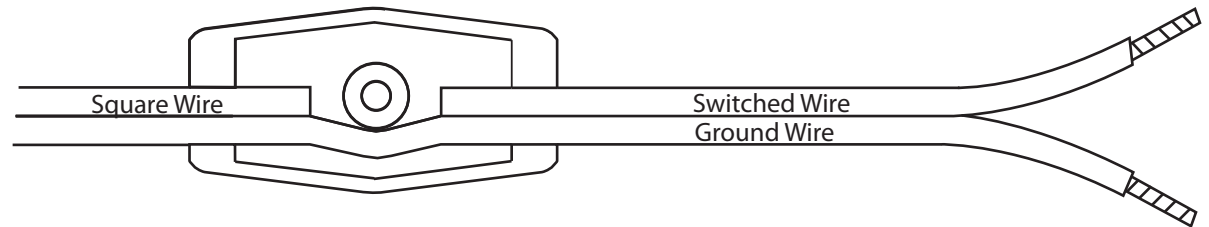


LAMP CIRCUIT DIAGRAM

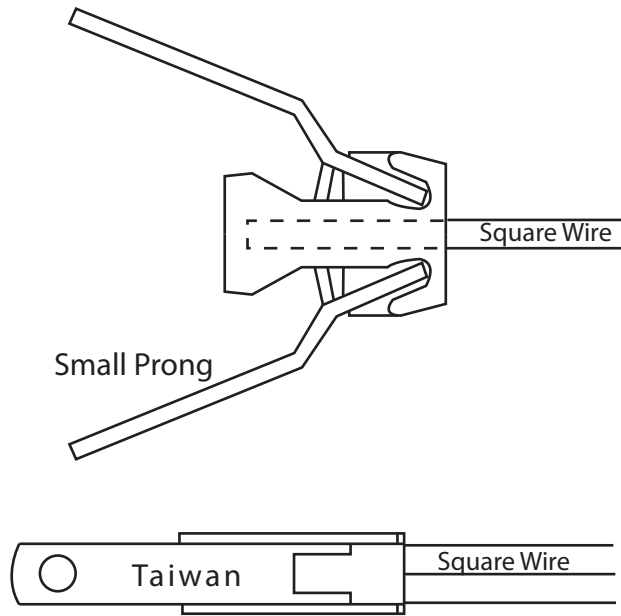

1 Step One

Hold the plug with the small prong facing you. Then insert the wire into the plug, with the square side facing up. Be sure to push the wire in all the way.

Then squeeze the prongs together, and slide the plugs cover onto the prongs. Make sure to press the plug together fully.

2 Step Two

Cut a 1/2" section out of the square wire, be careful to not cut into the other wire.

Unscrew the switch, and place the wire into the switch. The uncut wire goes around the top of the screw hole.

3 Step Three

Use the wire cutters to cut between the two wires and then separate the two halves.

Use wire strippers to strip approximately 1/2" of the plastic coating off the end of each wire. Using the 14 AWG slot.

Twist the wires tightly together.